

[DESIGN CENTERS](#)


[TOOLS & LEARNING](#)

[COMMUNITY](#)

[EDN VAULT](#)

[About Us](#)

[Sign In](#) | [Sign Up](#)

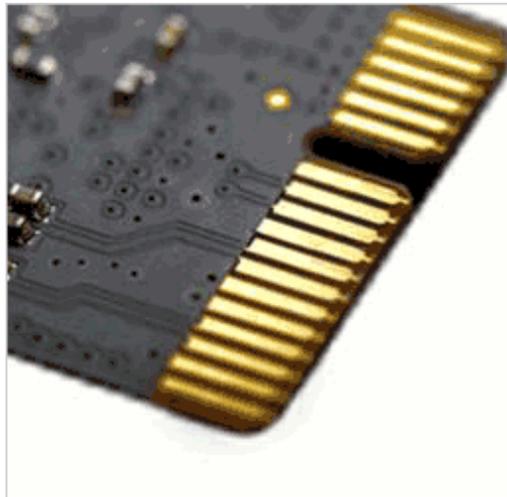

Connectors for Smaller, Faster Design

[Learn More >](#)

Sponsored by [Arrow.com](#)

[Home](#) > [Consumer Design Center](#) > [How To Article](#)

Loudspeaker operation: The superiority of current drive over voltage drive

Esa Merilainen -October 22, 2013

24 Comments

Share

5



Tweet

Like 0

This is an overview of the destructive effects that voltage drive has on the performance of electrodynamic loudspeakers. A more comprehensive treatment of the subject can be found in the book *[Current-Driving of Loudspeakers: Eliminating Major Distortion and Interference Effects by the Physically Correct Operation Method](#)* by Esa Meriläinen.

Today, practically all available audio amplifier and loudspeaker equipment works on the voltage drive principle without significant exceptions. This means that the power amplifier acts as a voltage source exhibiting low output impedance and thus strives to force the voltage across the load terminals to follow the applied signal without any regard to what the current through the load will be.

However, both technical aspects and listening experiences equally indicate that voltage drive is a poor choice if sound quality is to be given any worth. The fundamental reason is that the vague electromotive forces (EMF) that are generated by both the motion of the voice coil and its inductance seriously impair the critical voltage-to-current conversion, which in the voltage drive principle is left as the job of the loudspeaker.

The driving force (F), that sets the diaphragm in motion, is proportional to the current (I) flowing through the voice coil according to the well known formula $F = BIl$ where the product BI is called force factor (B = magnetic flux density; l = wire length in the magnetic field). B is the flux density that exists when the current is zero. (The current always induces its own magnetic field, which may react with adjacent iron, but the effect is not related to this equation.)

This force, then, determines the acceleration (A) of the diaphragm, which in the main operation

area (the mass-controlled region) is got from the Newtonian law $F = mA$. The radiated pressure, in turn, follows the instantaneous acceleration and not the instantaneous displacement, as many mistakenly imagine.

The most remarkable thing here regarding loudspeakers is that the voltage between the ends of the wire does not appear anywhere in these equations. That is, the speaker driver in the end obeys only current, not caring what the voltage across the terminals happens to be.

There cannot be found any scientifically valid reasons that justify the adoption of voltage as the control quantity - it is only due to the historical legacy originated almost a century ago, most likely by cheapness and simplicity; the quality and physical soundness of operation have not been considerations in this choice. Engineers are also more accustomed to identifying electrical signals as voltages rather than currents.

At least the hi-fi community should be interested and able to better see through this discrepancy. But they too have taken the state of affairs as a given, being largely conditioned to the wishful thinking that tightly held voltage somehow "controls cone motion," even up to middle and high frequencies. Such a notion doesn't have real scientific grounds, and it can be clearly shown by basic analysis and modeling that any damping effects that voltage drive can have on driver operation are strictly limited to the bass resonance region.

The components of impedance

The electrical equivalent circuit of a moving-coil drive unit can be depicted as the series connection of a resistor and two voltage sources, as shown in Figure 1. R_c represents the voice coil DC resistance; voltage source E_m represents the motional EMF (so-called back-EMF) of the driver and is calculated by $E_m = BIV$ (V = voice coil velocity); and voltage source E_i represents the inductance EMF that is generated by the lossy inductance of the voice coil. This is the proper and essential representation of the electrical system for examining the amplifier-speaker interface. Any

wiring resistances and possible output resistance of the voltage amplifier simply add to R_c and thus don't need any specific attention.

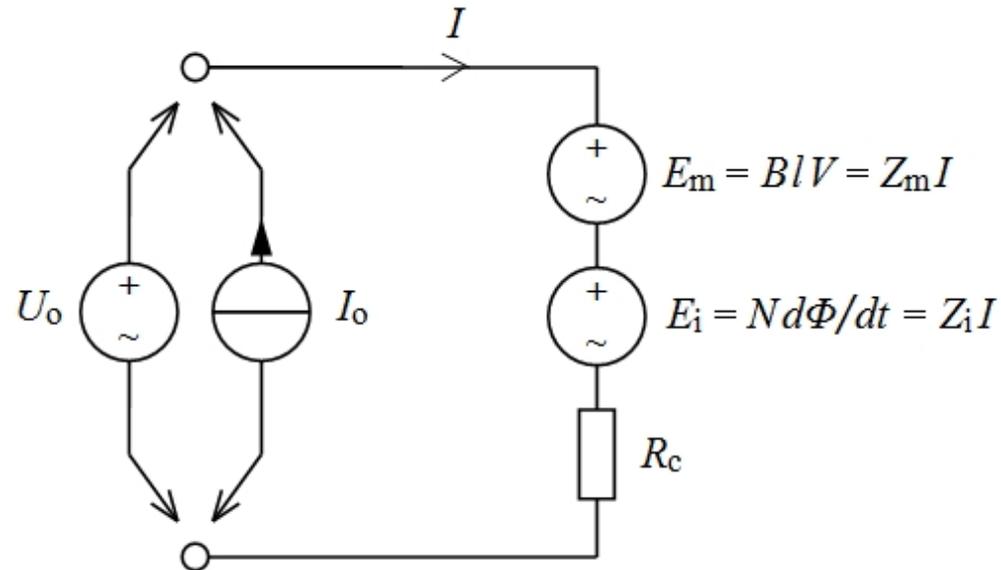


Figure 1: The electrical equivalent circuit of a moving-coil transducer with two kinds of feeding sources.

Both E_m and E_i are subject to a multitude of disturbances that corrupt the flow of current when the circuit is fed by a voltage source (U_o). Thus the magnitudes of these two are of utmost interest. When the feed comes from the current source (I_o), E_m and E_i only appear as additional voltages in the amplifier output, having no influence on the current.

In the impedance modulus curve of a typical moving-coil driver ($|Z_{tot}|$ in Figure 2), E_m manifests itself as the high peak at the resonant frequency, while E_i is responsible for the gradual rise typically starting in the whereabouts of 300 Hz. When looking at such a curve, one can easily be mistaken to assume that E_m is significant only near the fundamental resonant frequency or that E_i is significant only at the highest operating frequencies. In reality, however, these two components

are of almost opposite phase in the midrange and therefore largely mask each other near the impedance minimum.

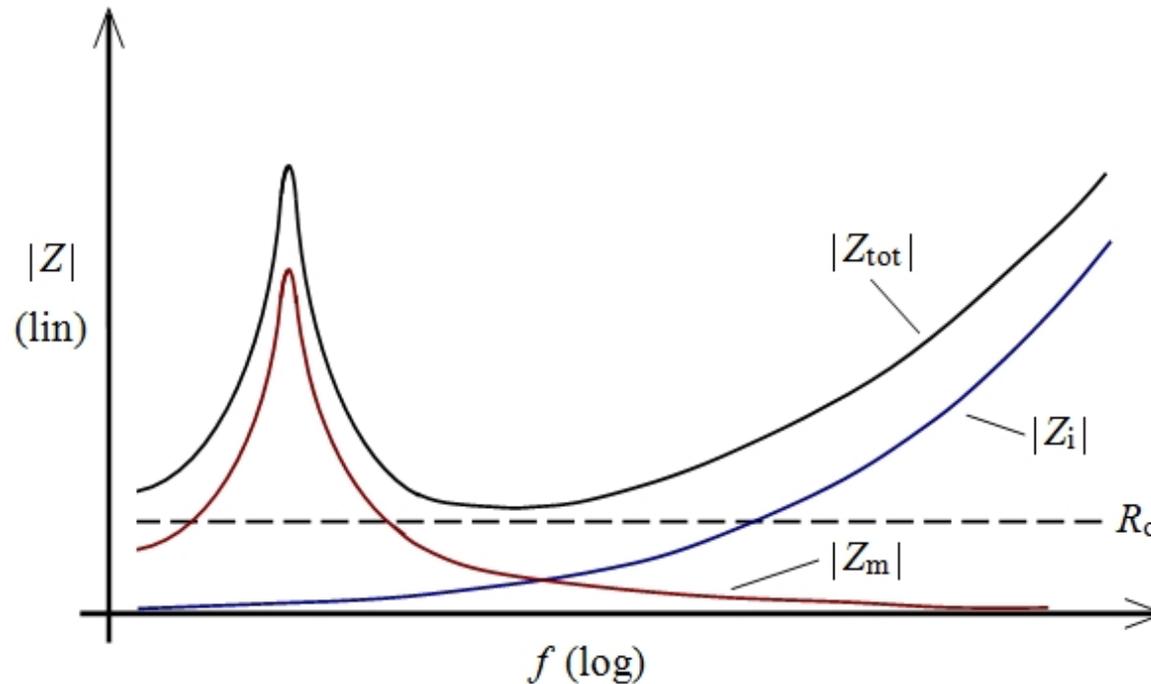


Figure 2: Composition of the impedance magnitude curve of a typical cone driver. Both the motional impedance Z_m and the inductance impedance Z_i have considerable magnitude throughout the main operation area.

Figure 2 thus also shows the actual and typical magnitudes of the impedance components separately, which are also measurable by special techniques. It is seen that the sum of $|Z_m|$ and $|Z_i|$ is in fact in the whole operation band at least of the same order of magnitude than R_c . Increasing driver efficiency also increases both $|Z_m|$ and $|Z_i|$.

Share

5

G+

Tweet

Like 0

Next: [Basic low-frequency operation](#)

< Previous Page 1 of 3 Next >

SPONSORED CONTENT



Comparing Our Favorite Home 3D Printers

With the increased accessibility of electronics, IoT applications, and DIY projects, 3D printers have exploded in popularity the last few years. With a 3D printer,

you can create three-dimensional objects to meet the demands of any project or simply satisfy your creative drive to build an objet d'art to display in your office, home, or lab.

Sponsored By [Arrow.com](#)

□

24 Comments

Write a Comment

Submit Comment

To comment
please [Log In](#)



TedC

No speakers is actually driven from a voltage source anyway, they're driven through a complex passive network that used to be the crossover but which is now a compensator also.

Aug 2, 2016 12:42 PM EDT

0 | 2

[Reply](#)



Michael Dunn

Lots of speaker drivers are driven from a voltage source. E.g., in my own bi-amped, electronically crossed-over boxes. And many professional studio monitors...

Aug 2, 2016 2:04 PM EDT

0 | 0

[Reply](#)



TedC

A speaker will sound best when driven from the source

impedance it was designed for.

Aug 2, 2016 12:39 PM EDT

👍 0 | 🗑️ 1

[Reply](#)



bcarso

Having obtained the book, I strongly recommend it.

Brad

Feb 9, 2014 2:29 PM EST

👍 0 | 🗑️ 0

[Reply](#)



Mark Spellman

Current drive of speakers was actually quite common back in the day of pentode output stages with no feedback. This was typical of "all American" five tube radios and low priced record players. With the pentode's high output impedance (AKA current source), the rising impedance of the speaker at high frequencies caused an unwanted treble boost which was compensated for by adding a "tone condenser" across the primary of the output transformer.

I agree about damping factor being a load of nonsense.

My theory is that it was popularized by solid state amplifier marketers in the 1960s who wanted a number to "prove" the superiority of their product.

Oct 30, 2013 2:08 PM EDT

 1 |  0

[Reply](#)



timofey

You are right, tube amplifiers have high output impedance and produce a different sound with the same loudspeakers. In my country in seventies there was a special term - "transistor sound" stressing that the same loudspeaker usually sounds worse when it is driven from a semiconductor (i.e. voltage-feedback) amplifier. The new usually turns out to be something old but forgotten. The first article offering "current drive" of loudspeakers I saw about 30 years ago. As usual - the new turns out to be the old but forgotten.

Oct 31, 2013 1:46 AM EDT

 1 |  0

[Reply](#)



JeffL_2

Oh and one more thing, applying negative feedback

around an amplifier to reduce distortion has the mathematical tendency to LOWER the output impedance. This would mean the last voltage-to-current conversion stage would have to operate without benefit of negative feedback to remain a high-impedance current source, so the measured distortion level of such an amplifier would be higher, not generally a desirable situation in an audio system.

Oct 25, 2013 7:01 PM EDT

0 | 0

[Reply](#)



Esa Merilainen

In current-output (transconductance) amplifiers, the feedback represents the current flowing through the load and thus increases the output impedance while reducing distortion similarly as with voltage feedback. The two forms of feedback can also be mixed to adjust the output impedance.

Yes, for a given load impedance and signal level, current-drive needs some extra voltage margin especially with highly complex loads; but on the other hand, the peak current demand is correspondingly lower and precisely known.

Applying pure current-drive for existing voltage speakers is not so advisable due to frequency response alteration. Speakers naturally have to be designed for the concept, preferably beginning from the drivers.

Oct 26, 2013 1:27 PM EDT

👍 0 | 🗨️ 0

[Reply](#)



JeffL_2

If I think really hard I do remember seeing current feedback applied around a transconductance amp once upon a time but that was DECADES ago (!), I'm pretty sure the application was a torque motor drive so I'm sure the topic of "distortion" never came up. The premise of applying large amounts of feedback around a load with a highly complex reactance is bad enough, include varying amounts of back EMF and I have a feeling you'll have a hard enough time trying to "establish" stability, may not leave you with enough "degrees of freedom" to worry much about how much the feedback improves

linearity. (I don't recall even seeing a bipolar OTA between the time I saw that old circuit and now, all I seem to run into are unipolar adaptations on the theme of current mirrors.) I'll more than accept that your "premise" is correct (in fact it HAS to be) but like you were hinting at the difficulty is in making it work. Also if you have to drive a loudspeaker coil through an essentially undamped resonance impedance peak you WOULD need all kinds of compliance to keep the current going, so I think the concept really makes more sense in something like a powered speaker system. Thanks for the comment.

Oct 26, 2013 2:21 PM EDT

👍0 | 🗑️0

[Reply](#)



Jacec

You can build a spice simulation circuit and check that this story is simply untrue. The distortions lower regardless of feedback type. I use currently Esa M. invented audio set and it cannot be compared with even the best traditional sets (it resembles little bit old tube radio sound but it is far

better)

Jacek

Mar 14, 2014 5:38 PM EDT

 0 |  0

[Reply](#)



Simon7382

Unless of course one applies current feedback instead of voltage feedback which actually increases the output impedance.

Dec 18, 2015 10:28 PM EST

 0 |  0

[Reply](#)



JeffL_2

All well and good, but if you consider primarily analog amplifier implementations and you require that the compliance voltage available to the cone's transducer be relatively high, the electrical efficiency becomes low and you wind up wasting lots of power in the pass devices a bit problematical when you're trying to deliver a kilowatt or more for doing sound reinforcement for an arena. This would also create havoc in any existing system with passive crossovers designed for voltage supply. Maybe someone besides myself remembers the

old transformer-based "25 volt" and "70.7 volt" distribution systems (all long out of service I suppose), they wouldn't work either (again not a big issue, just showing why things are like they are). I'm not sure how you could design an efficient digital PWM-based current drive, maybe someone can provide a circuit or reference for review?

Oct 25, 2013 3:27 PM EDT

 0 |  0

[Reply](#)



EMCgenius

25 and 70.7 volt systems are alive and well, but generally not seen in consumer equipment. These standards are used in public address systems, which is a different world.

Oct 29, 2013 1:15 PM EDT

 0 |  0

[Reply](#)



JCreasey

I think there are complexities with both voltage and current drive (and we certainly have gotten good at compensating for them in amplifier design) that could be corrected with direct motional feedback. Philips

championed this in the 70's and with today's SOCs, accelerometer sensors, new cone materials and rare earth magnets it should be possible to visit this again and produce much better low distortion mid/low range loudspeakers at reasonable costs.

Oct 24, 2013 2:10 PM EDT

0 | 0

[Reply](#)



timbalionguy

This is interesting, and may explain a significant difference I heard in a demonstration of different kinds of opamp-based headphone drivers. One opamp system was a traditional voltage system, the other a 'transconductance' system, if I recall.

Damping factor does help, and I have heard the audio quality improvement that happens when you drive a simple, relatively inexpensive loudspeaker system with a very large power amplifier.

This may also explain the good sound obtained from planar and plasma speakers, where the inertial mass of the driver is negligible.

But at the end of the day, I suspect that current drive will have its limitations and idiosyncrasies as well. There is no 'free lunch' when driving something as electromechanically complex as a loudspeaker.

What may be needed is some sort of mechanical feedback to tell the amplifier what the speaker is doing, and to correct it as needed. This has been tried before, and was marketed as a brand of (professional entertainment) speaker called 'servo drive'. I am told that these speakers had remarkable performance (apparently, especially for bass), but a few folks did not like how they sounded.

Oct 23, 2013 5:33 PM EDT

0 | 0

[Reply](#)



Douglas.Butler

When I was in college about 1980 there was a large speaker in the acoustics lab that used a high frequency LVDT for closed loop position control of the cone. I never heard it but I was told it performed well physically but "sounded terrible".

Oct 30, 2013 8:13 AM EDT

0 | 0

[Reply](#)



Rosalfonso Bortoni

Current-driven loudspeakers, when well designed, are indeed superior over the voltage-driven ones.

I would suggest the reading of this paper "Effects of Acoustic Damping on Current-Driven Loudspeakers," <http://www.aes.org/e-lib/browse.cfm?elib=14058>, and its references.

Also, Professor Hawksford has worked on this subject a long time ago, http://www.essex.ac.uk/csee/research/audio_lab/mal_colms_publications.html.

Oct 23, 2013 4:42 PM EDT

👍 0 | 🗑️ 0

Reply



Michael Dunn

For a given driver, designed to be as flat as possible under voltage drive, wouldn't the frequency response get messed up using current drive?

Oct 22, 2013 9:50 PM EDT

👍 0 | 🗑️ 0

Reply



catraeus

Exactly, Michael! These are all linear phenomena. It is all about equalization. The speaker has significant power converted to audio energy (the point, of course) which is the transduction from electrodynamic to acoustic domains. This power transduction has a transfer function vs. frequency which has been accommodated (over the course of the very same century) to produce some very fine sounds.

In my opinion, the majority of distortion is due to the excursion of the cone and its mechanical framework leading to these non-linear effects.

Oct 23, 2013 4:36 PM EDT

👍 0 | 👎 0

[Reply](#)



emover

And that is precisely the problem. The creation of pressure waves from typical loudspeaker is only a linear function during small excursions and the system has mechanical dampening built in. Fluid function changes and atmospheric variables will create an active

impedance match between the motor and the air. The effect can be a voltage standing wave reflection that could be difficult for a current source amplifier to stabilize (reactive EMF from normalizing the EM field). I agree that $BLV = Z_{ml}$ in an unloaded system, but not in a reactive environment.

Oct 30, 2013 3:20 PM EDT

 0 |  0

[Reply](#)



Amcfarl

I understand that Linn Products in the UK make (or made) a super-woofer with current drive and an accelerometer mounted on the cone to give feedback. Maybe someone has some info as to how well this worked?

NB the references to Bortoni et al do not work

Oct 30, 2013 3:45 PM EDT

 0 |  0

[Reply](#)



Jacec

In current-driving amp typically is in use a feedback resistor in series with load.

Action of this resistor can be compare to 'accelerometer'.

Mar 15, 2014 5:57 PM EDT

0 | 0

[Reply](#)



bcarso

Yes, agree with catraeus. Although there could be advantages to current drive, such as the near-elimination of voice-coil resistance-change effects with signal-induced self-heating, usually to take advantage of this requires that the loudspeaker has been developed using said current drive --- which no one does, at least for stand-alone loudspeakers. Otherwise simply applying current drive to a voltage-drive-derived loudspeaker is near-madness, and will result in huge frequency response anomalies.

There are several reasons for the nonlinear distortions in loudspeakers, including the suspension and airmass-loading departure from a linear relation of drive and displacement, and the change in the motor characteristic with displacement. At higher frequencies the sensitivity

will change as a function of voice coil position in the gap as well, but here the higher frequencies are not themselves moving the cone so much, but rather the sensitivity modulation from the low-frequency displacement entails intermodulation distortion. And IM distortion is by far the more audible and obnoxious effect, more likely to produce byproducts that are unconcealed by other desired material.

Of course another reason for the absence of significant current drive applications is the relative unfamiliarity of engineers with techniques of realizing it. But it can be done, and as Bortoni references, has been explored.

Timbalionguy mentions servo control, and indeed this is a valid and useful approach to reducing nonlinear distortions in woofers. An extension of this is to map the sensitivity as a function of displacement, for a broadband transducer, to the mids and highs, and "back out" the modulation effects. Many are the ways.

Brad

Oct 24, 2013 1:04 AM EDT

 0 |  0

[Reply](#)



Esa Merilainen

Besides the low-frequency implementation, that must be thought anew for current-drive, there is the obvious difference in responses that follows the driver's impedance curve. The response rises towards high frequencies when the voice coil inductance is no longer low-pass filtering (and also messing up) the current. The book also discusses various methods to compensate this effect in passive speakers where it can be an issue. In high-frequency units, the rise is often even beneficial, as the upper band limit can be pushed higher, and the power response becomes more even.

Oct 24, 2013 11:24 AM EDT

 0 |  0

[Reply](#)

Most Popular

Most Commented

5 great jokes about engineers

Fundamentals of USB Audio

Teardown: A tiny drone and its controller

10 drones you'll want to own

Teardown: Amazon Dash Button keeps you connected

Loudspeaker operation: The superiority of current drive over voltage drive

Negative feedback in audio amplifiers: Why there is no

such thing as too much

Appliance autonomy promises
to make life simpler

Bad-bulb finder fixes Christmas
lights

Teardown: WeMo Switch is
highly integrated

FEATURED RESOURCES

>> Micro BGA SMT Adapter- 0.5mm Pitch

>> Infineon solutions for Health and Fitness Devices

>> **Chip Fuse Protects Against Excessive Temperature & Overcurrent**

>> **Know the Difference Between an Inverter, Converter, Transformer and Rectifier**

>> **Dual Channel 4A, 42V, Synchronous Step-Down Silent Switcher 2 with 6.2µA Quiescent Current**

Subscribe to RSS:

or

DESIGN CENTERS

5G

Analog

Automotive

Components & Packaging

Consumer

DIY

IC Design

LEDs

Medical

PCB

Power Management

Sensors

Systems Design

Test & Measurement

MORE EDN

Blogs

Design Ideas

Tech Papers

Courses

Webinars

EDN TV

Events

About Us

ASPENCORE NETWORK

EBN EDN EE Times EEWeb Electronic Products Electronics-Tutorials Embedded Planet Analog ElectroSchematics
Power Electronics News TechOnline Datasheets.com Embedded Control Europe Embedded Know How Embedded News
IOT Design Zone Motor Control Design Electronics Know How

GLOBAL NETWORK

EE Times Asia

EE Times China

EE Times India

EE Times Japan

EE Times Taiwan

EDN Asia

EDN China

EDN Taiwan

EDN Japan

ESM China

Working With Us: [About](#) | [Contact Us](#) | [Media Kits](#)

[Terms of Service](#) | [Privacy Statement](#) | [Copyright ©2017 AspenCore All Rights Reserved](#)